

B.M.S. College of Engineering

(Autonomous Institution affiliated to VTU, Belagavi)

Bengaluru – 19

Department of Computer Science and Engineering



Verilog Program List

19CSPC34

Laboratory Manual

(AUTONOMOUS SCHEME 2019)

B.M.S. College of Engineering

(Autonomous Institution affiliated to VTU, Belagavi)

Bengaluru - 19

Department of Computer Science and Engineering



Laboratory Certificate

This is to certify that Mr. _____
_____ has satisfactorily completed the course of Experiments
in Practical _____ prescribed by the Department during the
year _____

Name of the Candidate: _____

USN No.: _____ Semester: _____

| Marks | |
|------------|----------|
| Max. Marks | Obtained |
| 10 | |

| Marks in Words | |
|----------------|--|
| | |

Signature of the staff in-charge

Head of the Department

Date:

B.M.S. College of Engineering

(Autonomous Institution affiliated to VTU, Belagavi)

Bengaluru - 19

Department of Computer Science and Engineering



Laboratory Certificate

This is to certify that Mr. _____
_____ has satisfactorily completed the course of Experiments
in Practical _____ prescribed by the Department during the
year _____

Name of the Candidate: _____

USN No.: _____ Semester: _____

| Marks | |
|------------|----------|
| Max. Marks | Obtained |
| 10 | |

| Marks in Words | |
|----------------|--|
| | |

Signature of the staff in-charge

Head of the Department

Date:

B.M.S. College of Engineering

(Autonomous Institution affiliated to VTU, Belagavi)

Bengaluru - 19

Department of Computer Science and Engineering



Laboratory Certificate

This is to certify that Mr. _____
_____ has satisfactorily completed the course of Experiments
in Practical _____ prescribed by the Department during the
year _____

Name of the Candidate: _____

USN No.: _____ Semester: _____

| Marks | |
|------------|----------|
| Max. Marks | Obtained |
| 10 | |

| Marks in Words | |
|----------------|--|
| | |

Signature of the staff in-charge

Head of the Department

Date:

B.M.S. College of Engineering

(Autonomous Institution affiliated to VTU, Belagavi)

Bengaluru - 19

Department of Computer Science and Engineering



Laboratory Certificate

This is to certify that Mr. _____
_____ has satisfactorily completed the course of Experiments
in Practical _____ prescribed by the Department during the
year _____

Name of the Candidate: _____

USN No.: _____ Semester: _____

| Marks | |
|------------|----------|
| Max. Marks | Obtained |
| 10 | |

| Marks in Words | |
|----------------|--|
| | |

Signature of the staff in-charge


Head of the Department

Date:

Verilog Program List

19CSPC34

Laboratory Manual
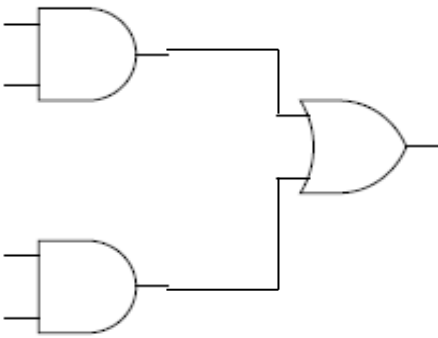
| Serial No. | Title |
|------------|---|
| | CYCLE I Structural Modeling |
| 1. | <p>Write HDL implementation for the following Logic</p> <p style="text-align: center;">a. AND/OR/NOT</p> <p>Simulate the same using structural model and depict the timing diagram for valid inputs.</p> |
| 2. | <p>Write HDL implementation for the following Logic</p> <p style="text-align: center;">a. NAND/NOR</p> <p>Simulate the same using structural model and depict the timing diagram for valid inputs.</p> |
| 3. | <p>Write HDL implementation for the following Logic</p> <div style="text-align: center;">  </div> <p>Simulate the same using structural model and depict the timing diagram for valid inputs.</p> |
| 4. | Write HDL implementation for a 4:1 Multiplexer. Simulate the same using structural model and depict the timing diagram for valid inputs. |
| 5. | Write HDL implementation for a 2-to-4 decoder. Simulate the same using structural model and depict the timing diagram for valid inputs. |
| 6. | Write HDL implementation for a 4-to-2 encoder. Simulate the same using structural model and depict the timing diagram for valid inputs. |

| | |
|-----|--|
| | |
| | CYCLE II Behavior Modeling |
| 7. | Write HDL implementation for a RS flip-flop using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs. |
| 8. | Write HDL implementation for a JK flip-flop using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs. |
| 9. | Write HDL implementation for a 4-bit right shift register using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs. |
| 10. | Write HDL implementation for a 3-bit up-counter using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs. |
| | CYCLE III Dataflow Modeling |
| 11. | Write HDL implementation for AND/OR/NOT gates using data flow model. Simulate the same using Dataflow model and depict the timing diagram for valid inputs. |
| 12. | Write HDL implementation for a 3-bit full adder using data flow model. Simulate the same using Dataflow model and depict the timing diagram for valid inputs. |

Verilog Program List-19CSPC34
SCHEME OF CONDUCT AND EVALUATION

CLASS: III SEMESTER

YEAR: 2019-20

EVALUATION SCHEME Tutorial Test: 1 hour

| Expt. No. | TITLE | Max. Marks | Marks Obtained | Signature |
|-----------|--|------------|----------------|-----------|
| 1. | K-Map and Quine Mcclusky Method | 2 | | |
| 2. | AND/OR/NOT | 3 | | |
| 3. | NAND/NOR | | | |
| 4. | Logic diagram | | | |
| 5. | Multiplexer | | | |
| 6. | Decoder | | | |
| 7. | Encoder | | | |
| 8. | RS | | | |
| 9. | JK | | | |
| 10. | Shift right | | | |
| 11. | Counter | | | |
| 12. | AND/OR/NOT – data flow | | | |
| 13. | 3-bit full adder | | | |
| | Test: Viva – 2 Marks + Writeup – 1 Mark + Execution – 2 Marks | 5 | | |
| | TOTAL MARKS | 10 | | |
| | | | | |

Verilog Program List-19CSPC34
Rubrics

| Sl.No | Criteria | Excellent | Good | Average | Poor | Max Score |
|--------------|--|-----------|------|---------|------|-----------|
| | | | | | | |
| A | Design & specifications | 1 | 0.5 | 0.25 | 0 | 1 |
| B | Expected output | 2 | 1 | 0.5 | 0 | 2 |
| | Record | | | | | |
| C | Simulation/ Conduction of the experiment | 3 | 2 | 1 | 0 | 3 |
| D | K-Map and Quine Mcclusky Method | 2 | 1 | 0.5 | 0 | 2 |
| Viva | | | | | | 2 |
| Total | | | | | | 10 |
| | | | | | | |

STRUCTURAL MODELING

Experiment 1

1. Write HDL implementation for the following Logic
 - a. AND/OR/NOT

Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (OR GATE GIVEN)

```
module or_gate(A,B,Y);
```

```
input A,B; // defines two input port
```

```
output Y; // defines one output port
```

```
or g1(Y,A,B);
```

```
/*Gate declaration with predefined keyword or representing logic OR, g1 is optional user  
defined gate identifier */
```

```
endmodule
```

```
module testor;
```

```
reg A,B;
```

```
wire x;
```

```
or_gate org(A,B,x);
```

```
initial
```

```
begin
```

```
A= 1'b0; B=1'b0;
```

```
#20
```

```
A= 1'b0; B=1'b1;
```

```
#20
```

```
A= 1'b1; B=1'b0;
```

```
#20
```


```
A= 1'b1; B=1'b1;
```

```
#20
```

```
$finish;
```

```
end
```

```
endmodule
```

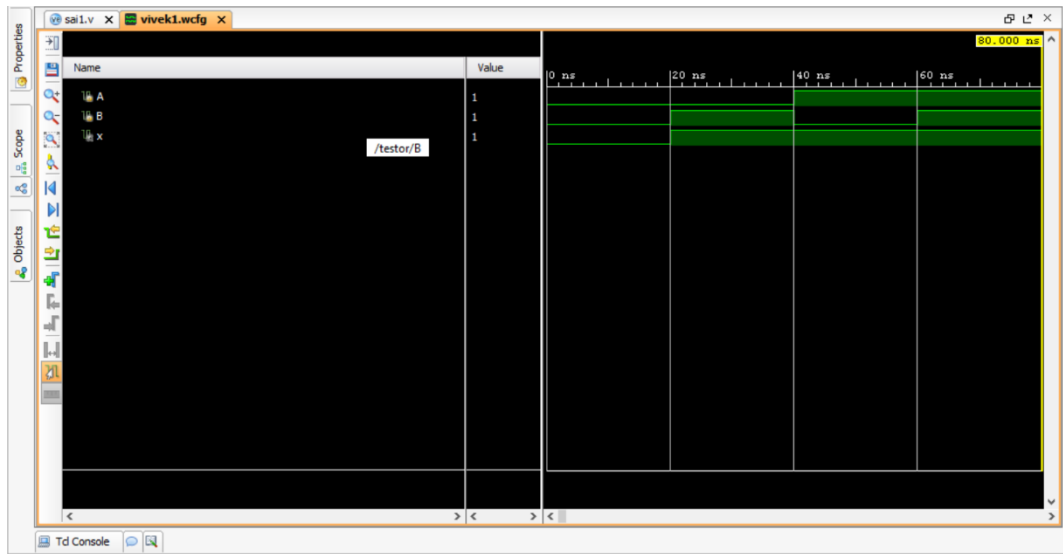

Experiment 2

Write HDL implementation for the following Logic

a. NAND/NOR

Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE(FOR NAND GATE)

```
module nand_gate(A,B,Y);  
input A,B;
```

```
// defines two input port
```

```
output Y;
```

```
// defines one output port
```


```
nand g1(Y,A,B);
```

```
endmodule
```

TEST MODULE


```
module testnand;  
reg A,B;  
wire x;  
nand_gate nandg(A,B,x);  
initial  
begin  
A= 1'b0; B=1'b0;  
#20  
A= 1'b0; B=1'b1;  
#20  
A= 1'b1; B=1'b0;  
#20  
A= 1'b1; B=1'b1;  
#20  
$finish;  
end
```

```
endmodule
```

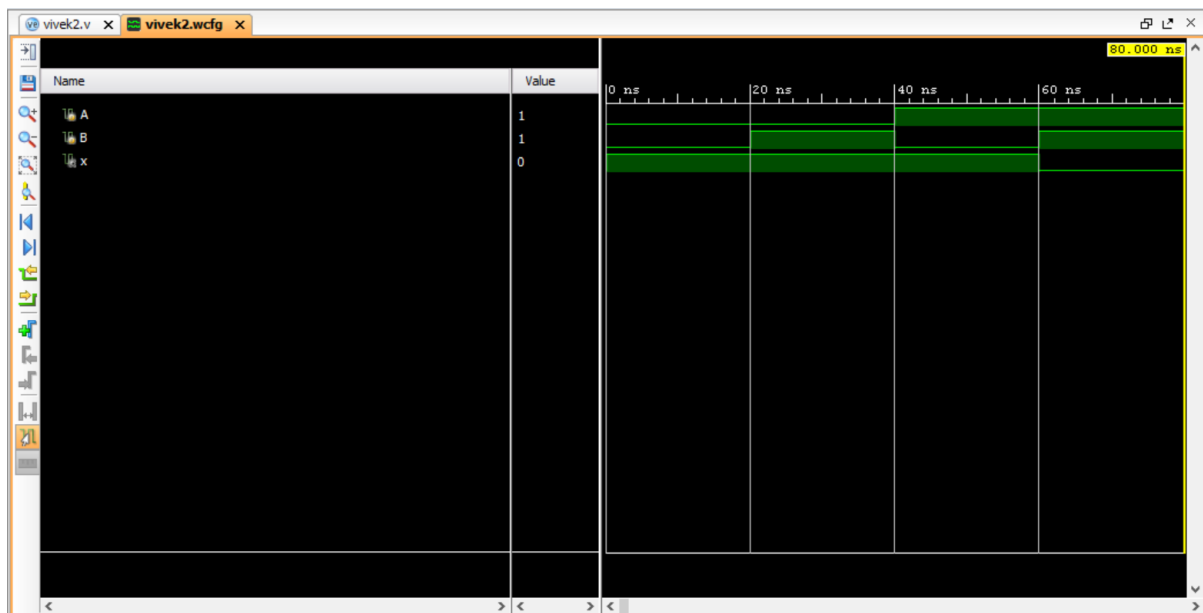

Experiment 3

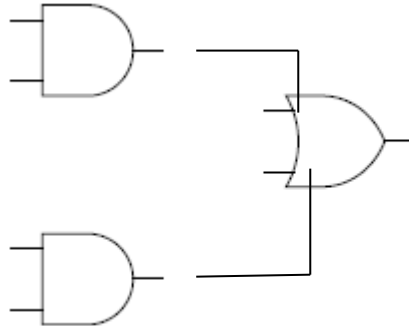Write HDL implementation for the following Logic




Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module addor(A,B,C,D,Y);  
input A,B,C,D;  
output Y;  
wire and_op1, and_op2;  
and g1(and_op1,A,B);  
and g2(and_op2,C,D);  
  
// g2 represents lower A.ND  
  
or g3(Y,and_op1,and_op2);  
  
// g3 represents the OR gate  
  
endmodule
```

TEST MODULE

```
module test andor;  
reg a,b,c,d;  
wire y;  
addor ao(a,b,c,d,y);  
initial  
begin  
a=0; b=1; c=1; d=1; #10  
a=0; b=0; c=1; d=0; #10  
$finish;  
end  
  
endmodule
```

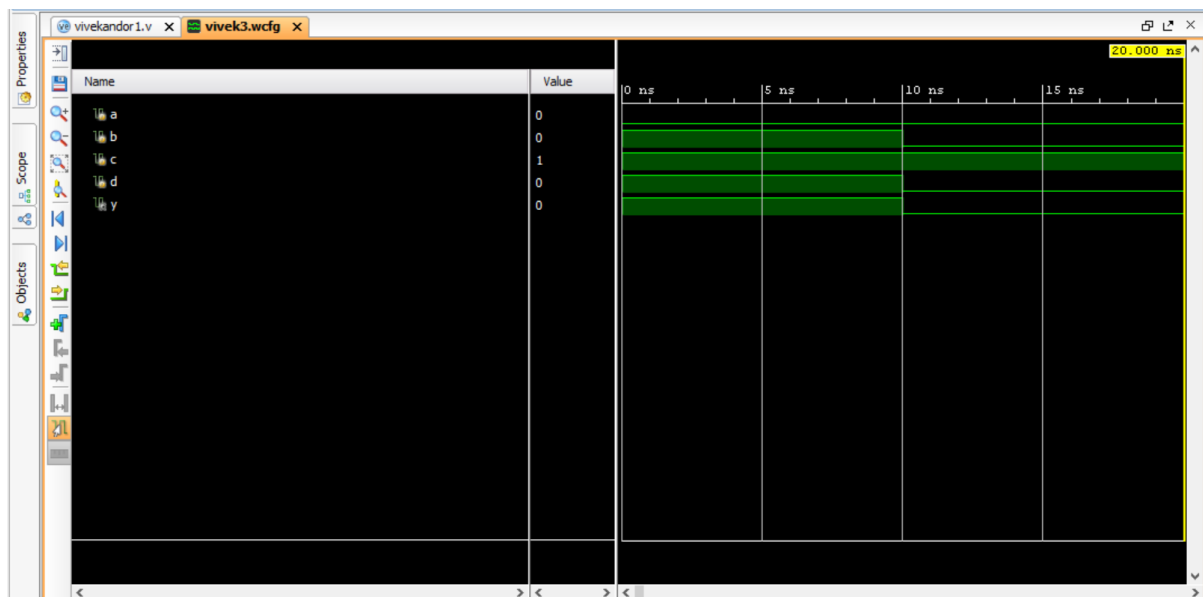

Experiment 4

Write HDL implementation for a 4:1 Multiplexer. Simulate the same using structural model and depict the timing diagram for valid inputs.


MAIN MODULE

```
module Multiplexer4to1(Do, Din, En);  
input En;  
input [3:0] Din;  
output Do;  
  
reg [1:0]Do;  
  
always @ (En or Din)  
begin  
if (En)  
begin  
case (Din)  
4'b0001: Do = 2'b00;  
4'b0010: Do = 2'b01;  
4'b0100: Do = 2'b10;  
4'b1000: Do = 2'b11;  
default: Do=2'bzz;  
endcase  
end  
end  
endmodule
```

TESTBENCH MODULE

```
module multiplexer_tb;  
reg [3:0] Din;  
reg En;  
wire Do;  
  
    Multiplexer4to1 mux(  
                                .Do(Do),  
                                .Din(Din),  
                                .En(En)  
                                );  
  
initial begin  
// Initialize Inputs  
En = 1;  
Din = 4'b0001; #100;  
Din = 4'b0010; #100;  
Din = 4'b0100; #100;  
Din = 4'b1000; #100;  
end
```

endmodule

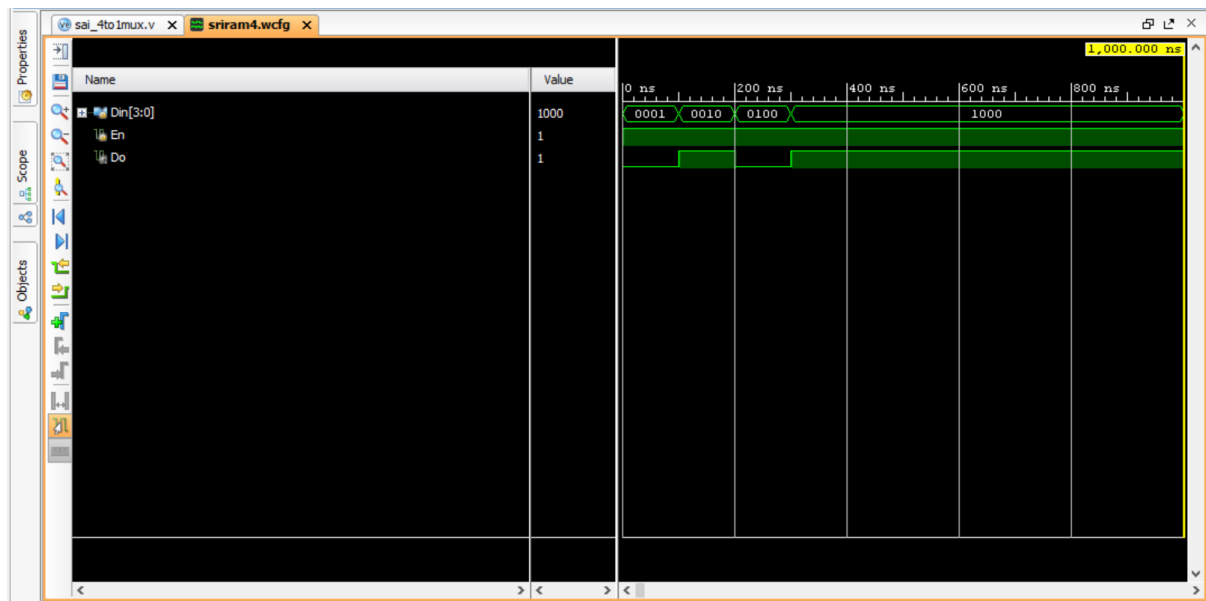

Experiment 5

Write HDL implementation for a 2-to-4 decoder. Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module decoder_case(Do, Din, En);
input En;
input [1:0] Din;
output [3:0]Do;

reg [3:0]Do;

always @ (En or Din)
begin
if (En)
begin
case (Din)
2'b00: Do = 4'b0001;
2'b01: Do = 4'b0010;
2'b10: Do = 4'b0100;
2'b11: Do = 4'b1000;


default: Do=4'bzzzz;
endcase
end
end
endmodule
```

TEST BENCH MODULE

```
module decoder_tb_v;
reg [1:0] Din;
reg En;
wire [3:0] Do;

decoder_case uut(
    .Do(Do),
    .Din(Din),
    .En(En)
);
initial begin
    // Initialize Inputs
    En = 1;
    Din =2'b00; #100;
    Din = 2'b01; #100;
    Din = 2'b10; #100;
```

```
Din = 2'b11; #100;  
end  
endmodule
```

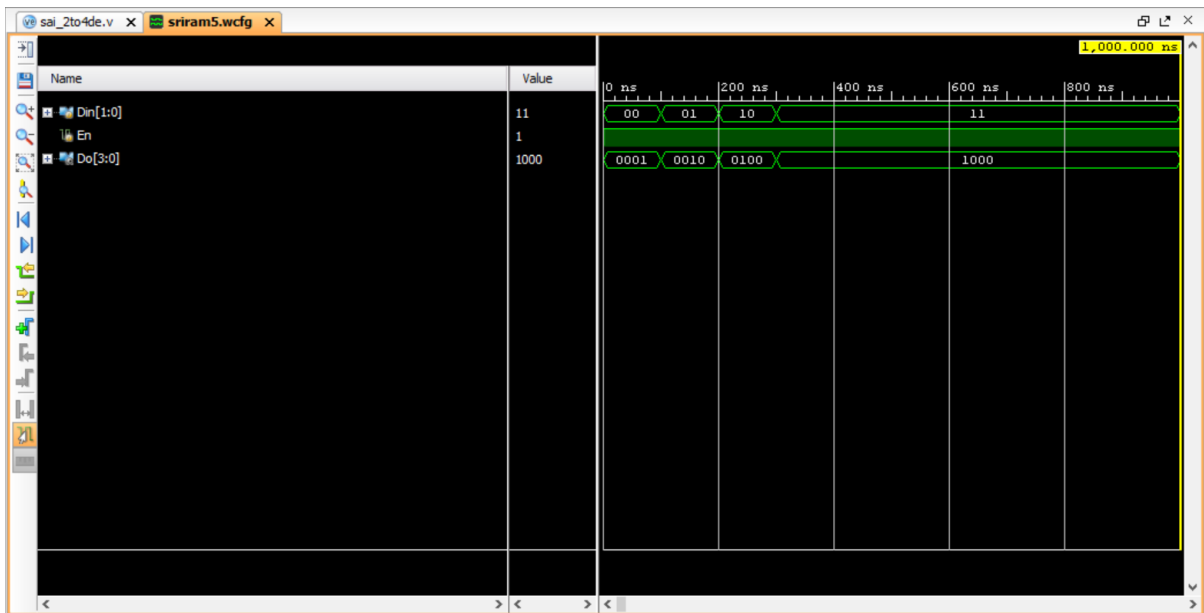

Experiment 6

Write HDL implementation for a 4-to-2 encoder. Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module Encoder(Do, Din, En);
input En;
input [3:0] Din;
output [1:0]Do;

reg [1:0]Do;

always @ (En or Din)
begin
if (En)
begin
case (Din)
4'b0001: Do = 2'b00;
4'b0010: Do = 2'b01;
4'b0100: Do = 2'b10;
4'b1000: Do = 2'b11;


default: Do=2'bzz;
endcase
end
end
endmodule
```

TESTBENCH MODULE

```
module encoder_tb_v;
reg [3:0] Din;
reg En;
wire [1:0] Do;

Encoder uut(
.D0(D0),
.Din(Din),
.En(En)
);
initial begin
// Initialize Inputs
En = 1;
Din = 4'b0001; #100;
Din = 4'b0010; #100;
Din = 4'b0100; #100;
```
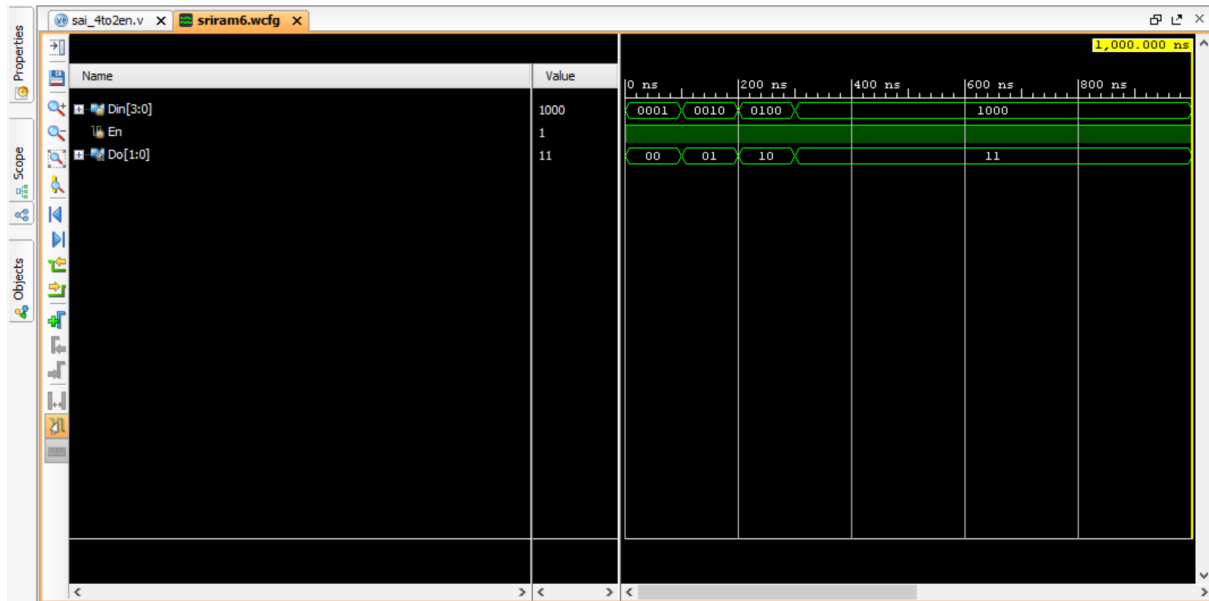
```
Din = 4'b1000; #100;  
end  
endmodule
```



BEHAVIOR MODELING

Experiment 7

Write HDL implementation for a SR flip-flop using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module SR_FF (sr, clk, q, qb);
input [1:0] sr;
input clk;
output reg q=1'b0;
output reg qb;
always @ (posedge clk)
begin
    case (sr)
        2'b00 : q = q ;
        2'b01 : q = 1'b0 ;
        2'b10 : q = 1'b1 ;
        2'b11 : q = 1'bz ;


    endcase

    qb =~ q;
end
endmodule
```

TEST MODULE

```
module testsrflipf;
reg [1:0] A;
reg c;
wire x, xb;
SR_FF srff(A,c,x,xb);
initial c=1'b0;
always #5 c=~c;
initial
begin

    A=2'b00; #10
    A=2'b01;#10
    A=2'b10;#10
    A=2'b11;
    #20 $finish;
end
endmodule
```

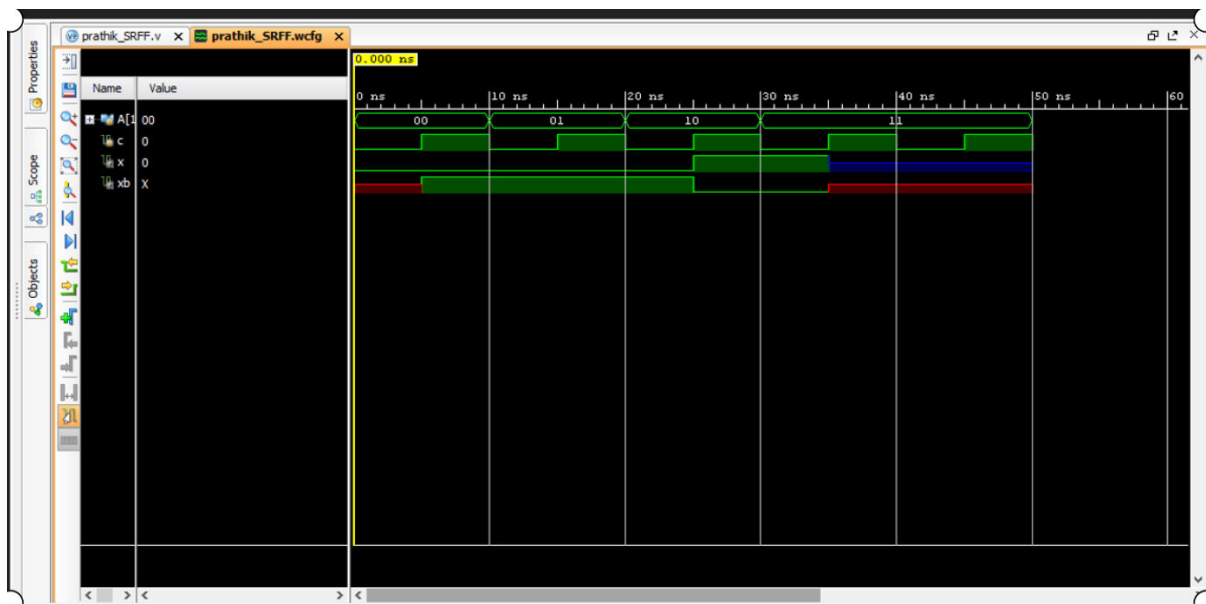

Experiment 8

Write HDL implementation for a JK flip-flop using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE


```
module JK_FF (jk, clk, q, qb);
input [1:0] jk;
input clk;
output reg q=1'b0;
output reg qb;
always @ (posedge clk)
begin
    case (jk)
        2'b00 : q = q ;
        2'b01 : q = 1'b0 ;
        2'b10 : q = 1'b1 ;
        2'b11 : q = ~q ;
    endcase
    qb =~ q;
end
endmodule
```

TEST MODULE

```
module testjkflipf;
reg [1:0] A;
reg c;
wire x, xb;
JK_FF jkff(A,c,x,xb);
initial c=1'b0;
always #5 c=~c;
initial
begin

    A=2'b00; #10
    A=2'b01;#10
    A=2'b10;#10
    A=2'b11;
    #20 $finish;
end
```

endmodule

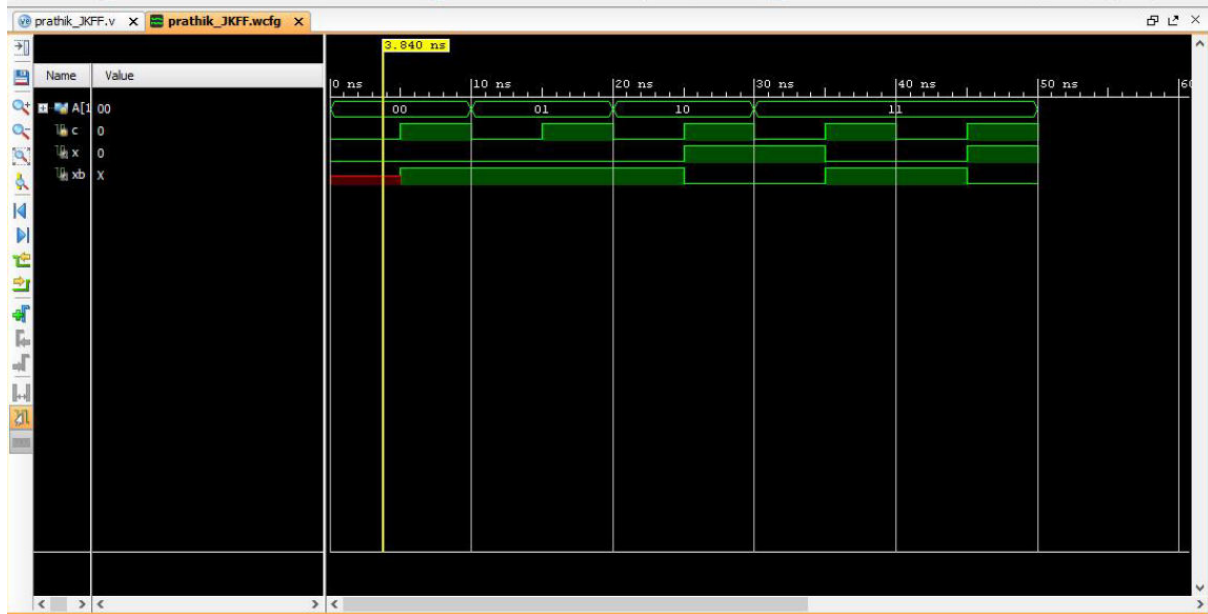

Experiment 9

Write HDL implementation for a 4-bit right shift register using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module Rshiftregister( input clk, input clrb, input SDR, output reg [3:0] Q );
//serial in, parallel out
    always @ ( posedge(clk), negedge(clrb))

        if (~clrb) Q<=4'b0000;
        else

            Q<={ SDR,Q[3:1]};
endmodule
```

TEST MODULE


```
module testRshiftregister;
    reg clk,clrb,SDR;
    wire [3:0]Q;

    Rshiftregister RS(clk, clrb, SDR, Q );
    initial
    begin

        clk =1;
        clrb=0;

        SDR=1;

        #100
        clrb=1;
        SDR=1;
        #150
        SDR=0;
        #200 $finish;
    end
    //initial and always run in parallel and starts its execution at 0ns
    always #5 clk=~clk;
endmodule
```

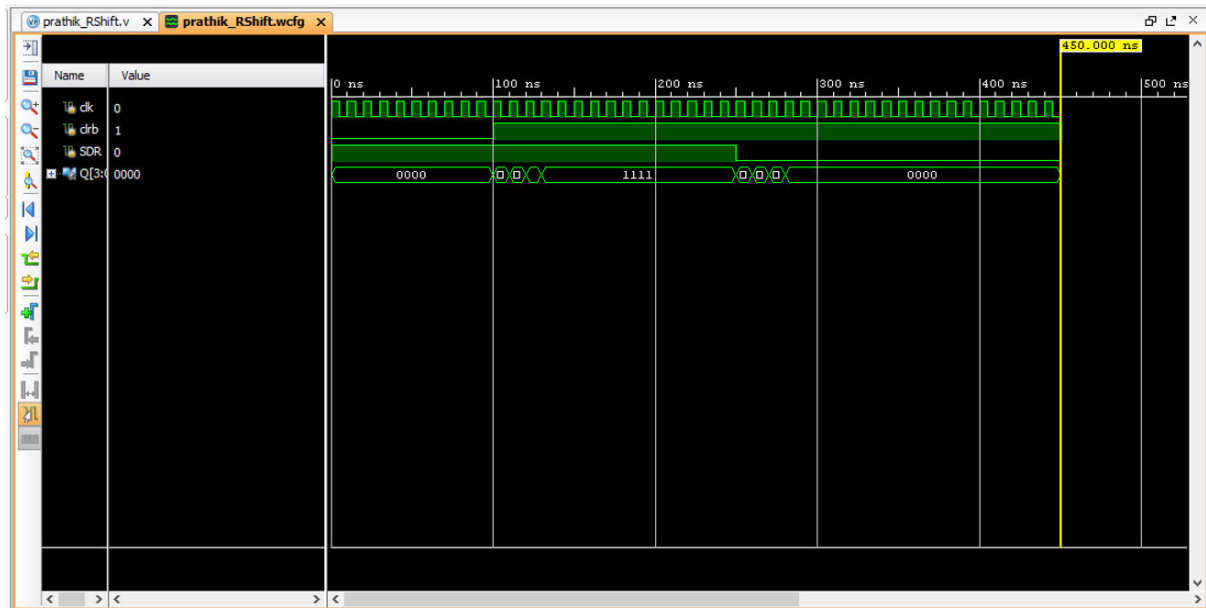

Experiment 10

Write HDL implementation for a 3-bit up-counter using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

Main Module

```
module counter_behav ( count,rst,clk);
input rst, clk;
output reg [2:0] count;
always @(posedge (clk))
if (rst)
count<= 3'b000;
else
count<= count + 1;
endmodule
```


TEST MODULE

```
module testmod;
reg r,c;
wire [2:0] ct;

counter_behav countbeh (ct,r,c);
initial
begin

    r =1;

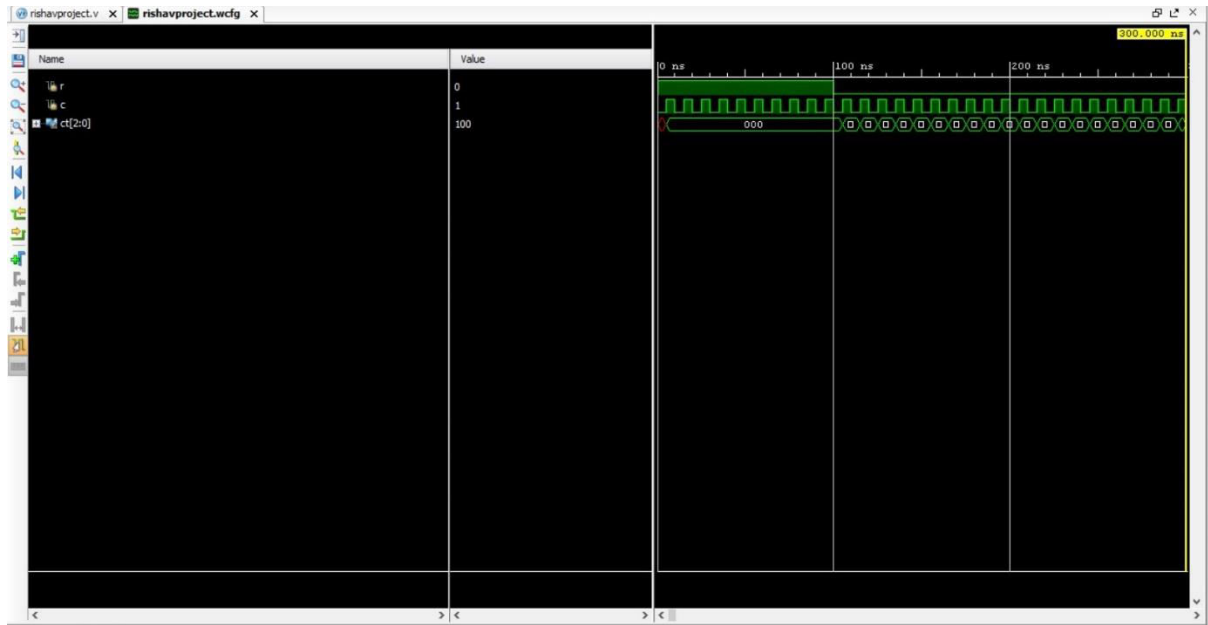    c=0;
    #100 r=0;
    #200 $finish;
end
//initial and always run in parallel and starts its execution at 0ns
always #5 c=~c;
endmodule
```



DATA FLOW MODELING

Experiment 11


Write HDL implementation for AND/OR/NOT gates using data flow model. Simulate the same using data flow model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module gates(input a, b, output [2:0]y);
    assign y[2]= a & b; // AND gate
    assign y[1]= a | b; // OR gate
    assign y[0]= ~a; // NOT gate
endmodule
```

TESTBENCH MODULE

```
modulegates_tb;
    wire [2:0]y;
    reg a, b;
    gatesdut(.y(y), .a(a), .b(b));
    initial
    begin
        a = 1'b0;
        b = 1'b0;
        #50;
        a = 1'b0;
        b = 1'b1;
        #50;
        a = 1'b1;
        b = 1'b0;
        #50;
        a = 1'b1;
        b = 1'b1;
        #50;
    end
endmodule
```

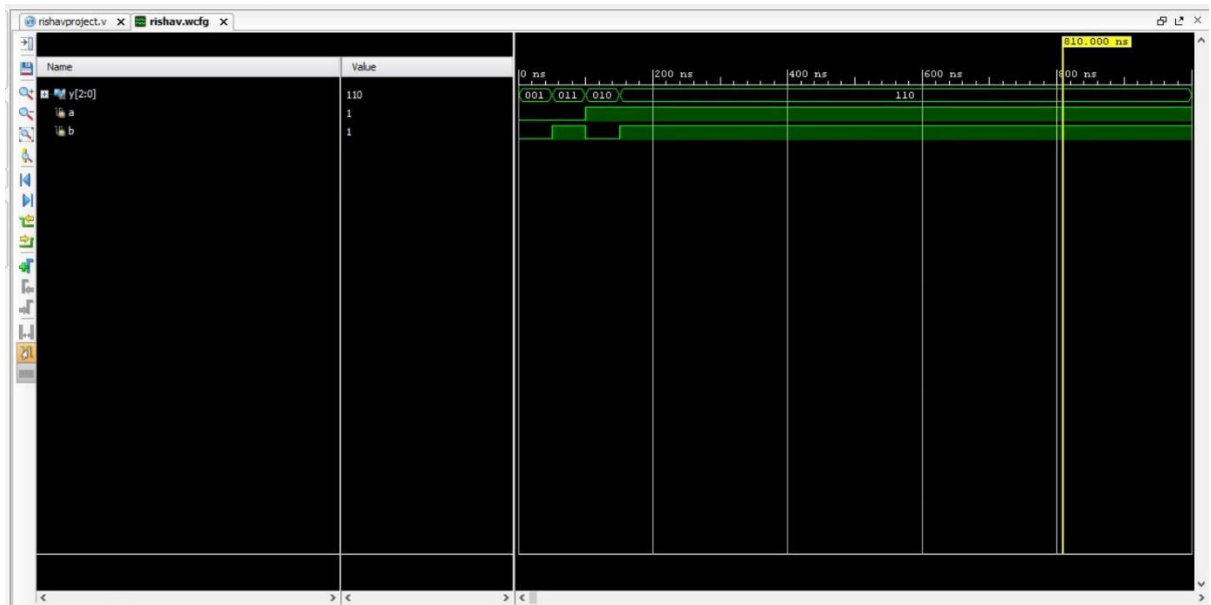

Experiment 12


Write HDL implementation for a 3-bit full adder using data flow model. Simulate the same using data flow model and depict the timing diagram for valid inputs.

MAIN MODULE

```
module fa(a,b,cin,s,cout);
    input a,b,cin;
    output s,cout;
    assign s = a^b^cin;
    assign cout = (a&b) | (b&cin) | (cin&a);
endmodule
```

TEST MODULE
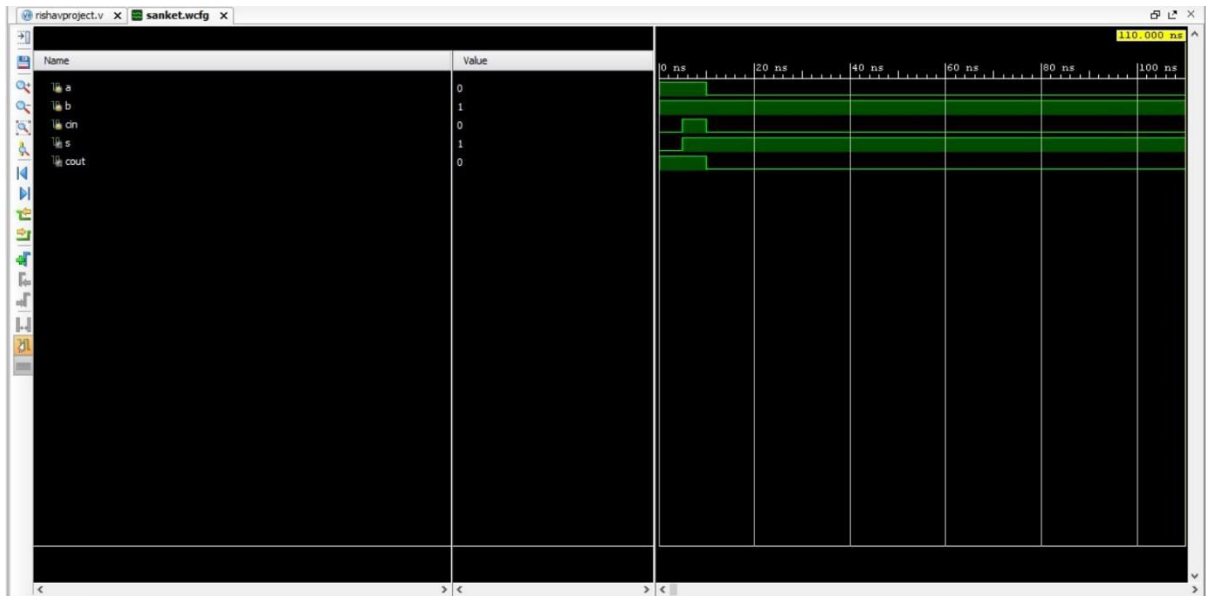
```
module fa_test;
    reg a,b,cin;
    wire s, cout;
    fa f1(a,b,cin,s,cout);
    initial
        begin
            a=1;   b=1; cin=0;
            #5
            a=1;   b=1; cin=1;
            #5
            a=0;   b=1; cin=0;
            #100 $finish;
        end
endmodule
```



Signature of the staff in-charge

